

CSE 251

Assignment - 03

Submitted by : Tasnim Rahman Moumita


ID : 22301689

Section : 18

Date of submission : 21. 04. 2024

Answer to the Question NO-01 (a)

Given,

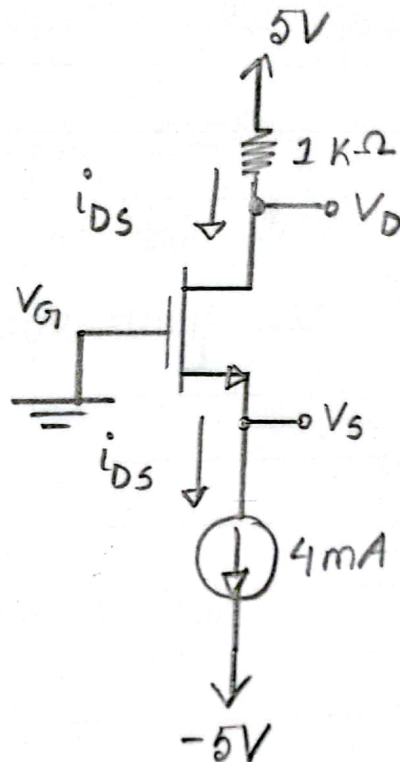

Given,

$$\begin{aligned} V_T &= 1\text{ V} \\ k &= k'_n \frac{W}{L} \\ &= 4\text{ mA/V}^2 \end{aligned}$$

Circuit : 1

$\therefore V_G$ is grounded.

$$\boxed{\therefore V_G = 0\text{ V}} \quad \underline{\underline{(Ans)}}$$

And,

According to KCL,

current that in the loop always remains same.

$\therefore i_{DS}$ will be equal as the current source.

$$\boxed{\therefore i_{DS} = 4\text{ mA}} \quad \underline{\underline{(Ans)}}$$

Answer to the Q. NO - 01 (b)

$$\therefore R_D = 1 \text{ k}\Omega \text{ [Given in the figure]}$$

This current through $1 \text{ k}\Omega = 10^3 \Omega$ resistor is equal as the drain-source current; since they are in series connection.

Here,

$$V_D = 5 \text{ V}$$

$$R_D = 1 \text{ k}\Omega \\ = 1 \times 10^3 \Omega$$

$$i_{DS} = 4 \text{ mA [from ('a')]} \\ = 4 \times 10^{-3} \text{ A}$$

Now,

Applying Ohm's Law,

$$i_{DS} = \frac{5 - V_D}{R_D}$$

$$\Rightarrow V_D = 5 - i_{DS} R_D$$

$$\Rightarrow V_D = 5 - (4 \times 10^{-3} \times 1 \times 10^3)$$

$$\Rightarrow V_D = 1 \text{ V}$$

$$\therefore V_D = 1 \text{ V}$$

(Ans.)

Answer to the Q. NO - 01 (c)

Let's assume,

$$V_S = x$$

Assuming that,

the MOSFET is in the Saturation Mode:-

$$\therefore i_D = \frac{K}{2} (V_{GS} - V_T)^2$$

Now,

$$V_{GS} = V_G - V_S$$

$$= 0 - x$$

$$[\because V_G = 0V]$$

$$\therefore \boxed{V_{GS} = -x \text{ V}}$$

Here,

$$\begin{aligned} V_{OV} &= V_{GS} - V_T \\ &= -x - 1 \end{aligned}$$

$$\therefore i_{DS} = \frac{K}{2} V_{OV}^2$$

$$\Rightarrow 4 = \frac{4}{2} (-x - 1)^2$$

$$\Rightarrow (-x - 1)^2 = 1$$

$$\Rightarrow x^2 + 2x + 1 = 0$$

$$\Rightarrow x^2 + 2x + 1 = 0$$

$$\begin{aligned} \text{Here,} \\ K &= 4 \text{ mA/V}^2 \end{aligned}$$

$$V_T = 1V$$

$$\begin{aligned} V_{OV} &= V_{GS} - V_T \\ &= -x - 1 \end{aligned}$$

$$V_G = 0V \text{ [from (a)]}$$

$$\therefore x = 0 \quad \text{or} \quad x = 2$$

$$\therefore V_S = -2 \quad \left[\because \text{We assumed,} \right. \\ \left. V_S = x \right]$$

$$\begin{aligned} \therefore V_{GS} &= V_G - V_S \\ &= 0 - (-2) \\ &= 2 > V_T \end{aligned}$$

$$\therefore V_{OV} = 1V$$

$$\begin{aligned} \therefore V_{DS} &= V_D - V_S \\ &= 1 - (-2) \\ &= 3V > V_{OV} \end{aligned}$$

\therefore our assumption is correct.

The MOSFET is in the saturation Mode.

$$\therefore V_S = -2V$$

(Ans.)

Ans. to the Q. NO-2

We know,

$$V_{SS} \frac{R_{on}}{R_L + R_{on}} < V_T$$

$$\Rightarrow 6 \times \frac{R_{on}}{5 + R_{on}} < 0.9$$

$$\Rightarrow 6 \times R_{on} < 0.9 (5 + R_{on})$$

$$\Rightarrow 6 \times R_{on} < (4.5 + 0.9 R_{on})$$

$$\Rightarrow 5.1 R_{on} < 4.5$$

$$\Rightarrow R_{on} < 0.8823 \text{ --- (i)}$$

Again,

$$R_{on} = \frac{1}{K'_n \frac{W}{L} V_{ov}}$$

$$\Rightarrow R_{on} = \frac{1}{\frac{W}{L}} \left(\frac{1}{K'_n V_{ov}} \right)$$

$$\Rightarrow R_{on} = \frac{L}{W} \times 4 \text{ --- (ii)}$$

\therefore from (i) & (ii) \Rightarrow

$$\frac{L}{W} \times 4 < 0.8823$$

$$\Rightarrow \frac{L}{W} < \frac{0.8823}{4}$$

$$\Rightarrow \frac{L}{W} < 0.2205$$

$$\boxed{\therefore \frac{W}{L} < 4.535}$$

(Ans.)

Given,

$$V_{SS} = 6V$$


$$V_T = 0.9V$$

$$R_L = 5k\Omega \\ = 5 \times 10^3 \Omega$$

$$K'_n V_{ov} = 0.25$$

Answer to the Q. NO - 03 (a)

Given figure,

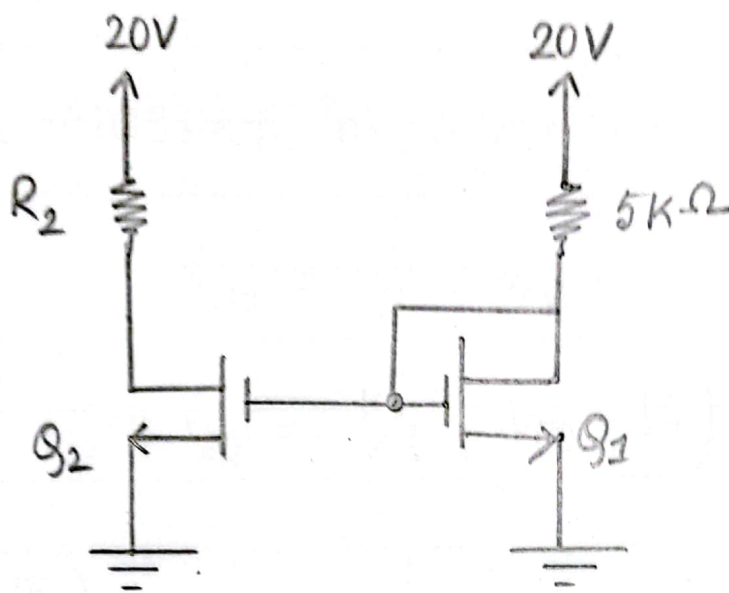

Given,

$$K'_n = 2 \text{ mA/V}^2$$

$$\frac{W}{L} = 2.5$$

$$V_T = 0.5 \text{ V}$$

As we know,

$$V_{DS} = V_D - V_S$$

$$V_{GS} = V_G - V_S$$

$$V_{OV} = V_{GS} - V_T$$

Now,

$$V_G = V_D$$

$$V_S = 0$$

$$\therefore V_{GS} = V_G = V_D$$

$$\therefore V_{DS} = V_G$$

Again,

$$V_{OV} = V_G - V_T$$

$$V_{DS} = V_G$$

$$\therefore V_{DS} > V_{OV}$$

\therefore The MOSFET is in the saturation mode.

(Ans:)

Answer to the Q. NO - 03 (b)

We know,

For a MOSFET in Saturation Mode,

$$i_{DS} = \frac{1}{2} K V_{OV}^2$$

$$\Rightarrow i_{DS} = \frac{K}{2} (V_{DS} - V_T)^2$$

Given,

$$K'_n = 2 \text{ mA/V}^2$$

$$\frac{W}{L} = 2.5$$

$$V_T = 0.5 \text{ V}$$

Here,

$$K = K'_n \left(\frac{W}{L} \right)$$

$$= 2 \times 2.5$$

$$\therefore K = 5$$

And, $V_{OV} = V_{DS}$ (which is at saturation edge)

Now, By applying KVL,
we get,

$$20 - 0 = 5 I_{D_I} + V_{DS}$$

$$\Rightarrow 20 = 5 I_{D_I} + V_D$$

$$\Rightarrow V_D = 20 - 5 I_{D_I} \quad \text{--- (1)}$$

$$\text{Now, } I_{D_I} = \frac{5}{2} (20 - 5 I_{D_I} - 0.5)^2$$

$$\Rightarrow I_{D_I} = \frac{5}{2} (19.5 - 5 I_{D_I})$$

$$\Rightarrow 2 I_{D1} = 5 \left\{ (19.5)^2 - 2 \times 19.5 \times 5 I_{D1} + (5 I_{D1})^2 \right\}$$

$$\Rightarrow 125 I_{D1}^2 - 977 I_{D1} - 5 \times (19.5)^2 = 0$$

$$\therefore I_{D1} = 3.658 \text{ mA}$$


$$I_{D1} = 4.157 \text{ mA}$$

$$\therefore \text{Now, } V_D = 20 - 5 (3.658) \\ = 1.71 \text{ V}$$

$$\therefore V_{GS1} = V_{GS2} = V_G$$

$$\therefore I_{D1} = I_{D2}$$

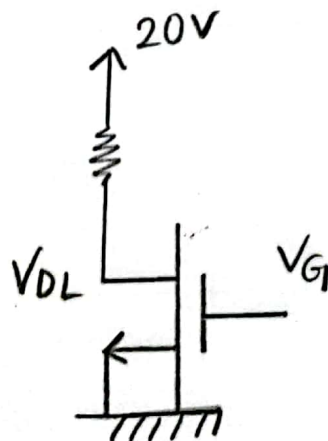And if we change V_{GS} ,
it will be like :-



$$\therefore I_{D1} = I_{D2} = 3.658 \text{ mA}$$

$$V_{DSL} = 20 - I_{D2} \times R_2$$

$$\Rightarrow 1.21 = 20 - 3.658 \times R_2$$

$$\Rightarrow R_2 = \frac{20 - 1.21}{3.658}$$

$$\therefore R_2 = 5.136 \text{ k}\Omega$$

(Ans:)

Here,

$$\therefore V_{DSL} = V_{GS} - V_T$$

$$\Rightarrow V_{DSL} = (1.71 - 0.5) \text{ V}$$
$$= 1.21 \text{ V}$$

Answer to the Q. NO-03(c)

Calculating the on-state resistance, R_{on} :- (for Q_2)


As we know,

$$V_{GS} = V_G - V_S$$

$$V_{OV} = V_{GS} - V_T$$

$$= (1.71 - 0.5) \text{ V}$$

$$= 1.21 \text{ V}$$

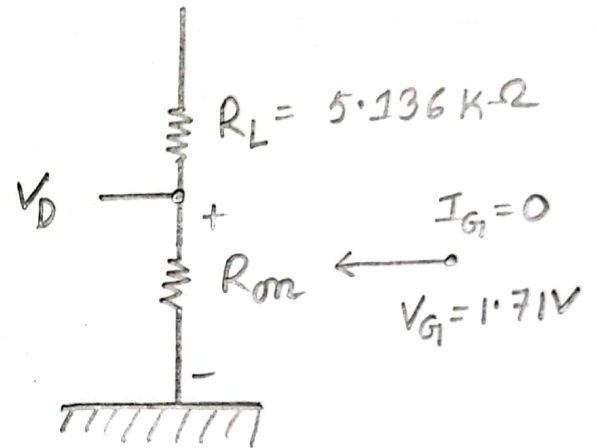

Again,

$$R_{on} = \frac{1}{K'_n \left(\frac{W}{L}\right) V_{OV}}$$


$$= \frac{1}{2 \times 2.5 \times 1.21}$$

$$\therefore R_{on} = 0.16529 \text{ k}\Omega$$


(Ans:)

Answer to the Q. NO-03(d)

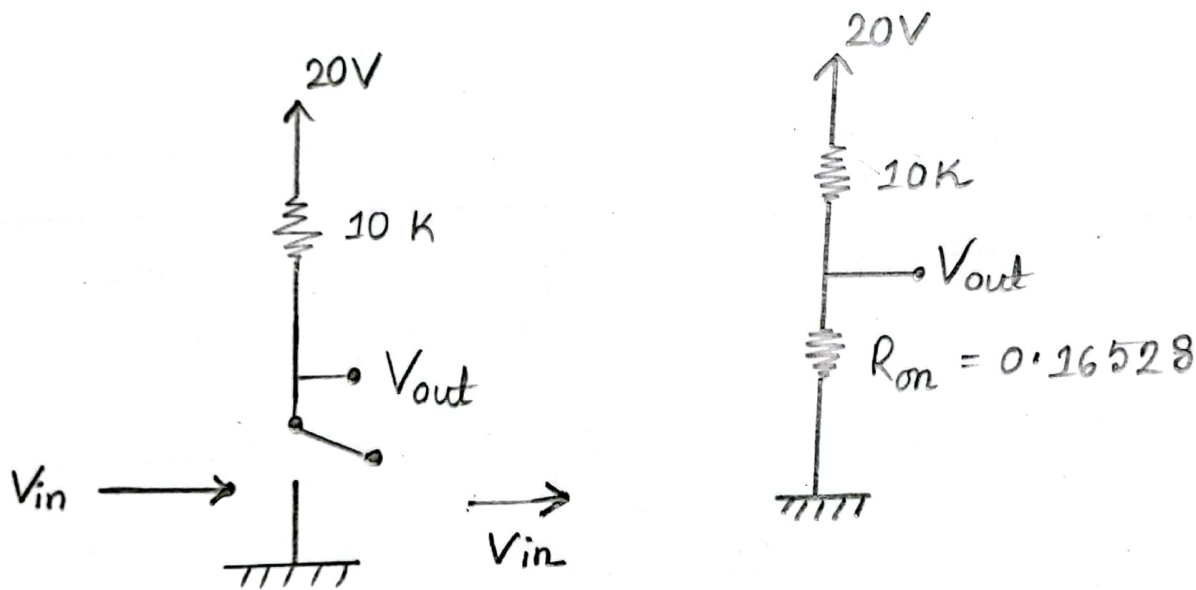Given,
an inverter is designed using Q_2 and a $10K$ resistor
Now,
drawing the circuits for better visualization;



\therefore VTC graph for the inverter:

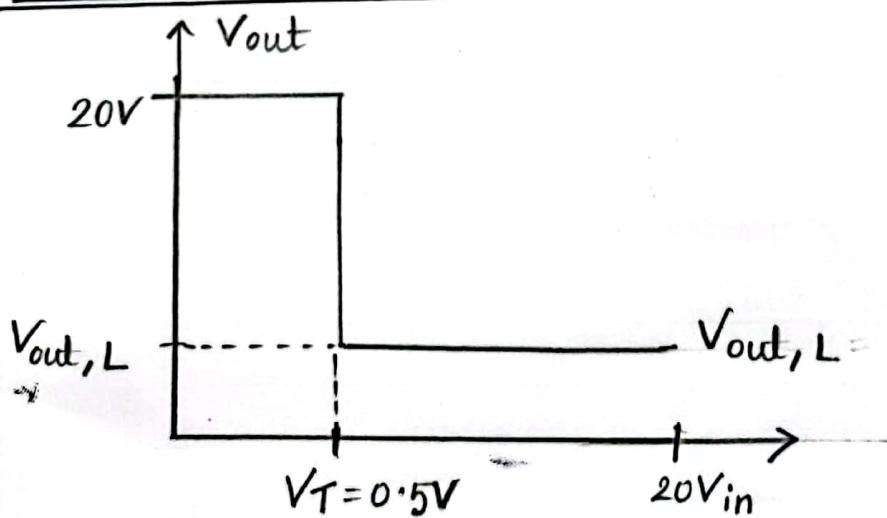

Now,

$$V_{out,H} = 20V$$

$$V_{out,L} = 20 \times \frac{0.1658}{0.16528 + 10}$$

$$= 0.3251V < V_T$$

Q Given function,

$$F = \overline{A\bar{B} + C}$$

Applying Morgan's Law:-

$$\overline{A\bar{B} + C} = \bar{A} \cdot \overline{\bar{B} \cdot C}$$

