

## Assignment 04


Total: 30

Deadline: 9 May, 2025

This assignment must be hand-written. Show ALL steps in ALL questions.


You do not need to submit the questions that are marked with 'Ungraded - Recommended for practice' as part of the assignment. Those are practice materials.

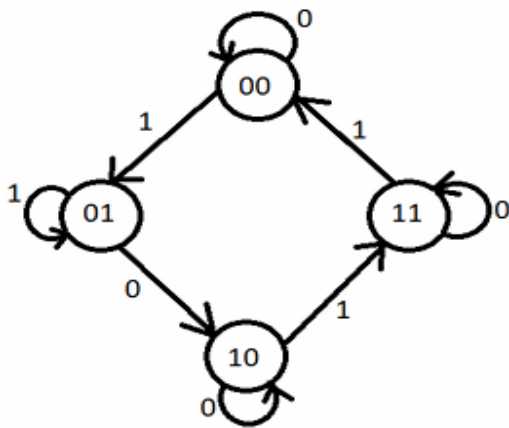1. [5 marks] Given the state diagram as follows, get the sequential circuit using **SR flipflop**.




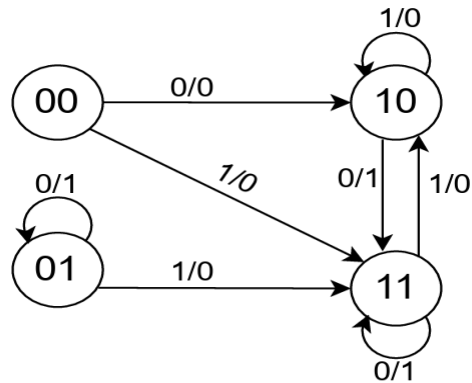2. [5 marks] Given the state diagram as follows, get the sequential circuit using


- SR flipflop [Ungraded - Recommended for practice]
- JK flipflop.



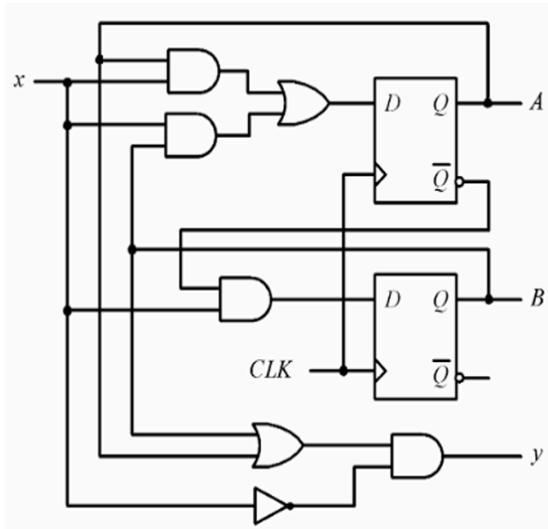3. [Ungraded - Recommended for practice]  
Draw the state diagram for the given circuit.



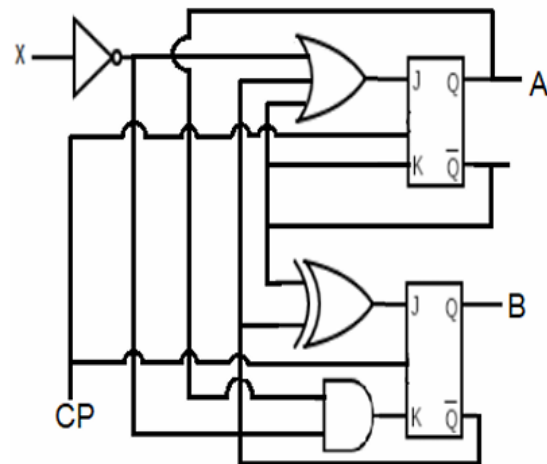4. [5 marks] Draw the state diagram for the given circuit.



## Assignment 04

Total: 30

**Deadline: 9 May, 2025**

**This assignment must be hand-written. Show ALL steps in ALL questions.**

**You do not need to submit the questions that are marked with 'Ungraded - Recommended for practice' as part of the assignment. Those are practice materials.**

5. [5 marks] Implement the following counter using **T flip flop**

**CSE110-> CSE111-> CSE220-> CSE221-> CSE331-> CSE221-> CSE321-> CSE110**

6. [5 marks] **3->4->6->10->12->13->15->3**

i. Implement the given counter using **JK flip-flop**.

ii. Implement the given counter using

**T flip-flop [Ungraded - Recommended for practice]**

**NB:** For states not given in the question, please move to the initial state as per the question.

7. [Ungraded - Recommended for practice]

Implement **4 bit up/down** counter using **JK flip-flop**

8. [Ungraded - Recommended for practice]

Implement the following counter using **JK FF**:  
**Green->Yellow->Red->Yellow->Green**

9. [5 marks] Implement the following counter using **JK FF**:

**1->2->3->5->7->11->13->1**