

CSE260 Lab Report 03

Group 03

Experiment Name:

Parity Generator and Checker

Submitted by,

Moumita Hossain, Group: 03

Id: 22301083, Section: 10,

Course: CSE260

Group Members:

1. Deb Aditya Barua, Id: 22301589
2. Moumita Hossain, Id: 22301083
3. Faiaz An Noor, Id: 22241092
4. Md Al Shariar Shisir, Id: 22301642

Department of Computer Science and Engineering
BRAC University
CSE 260: Digital Logic Design

Experiment # 3

Parity Generator and Checker

Objective:


- To design and implement an Even parity Generator and Even parity checker using XOR gates (IC-7486).

Required Components and Equipments


1. AT-700 Portable Analog/Digital Laboratory
2. 7400×3

Diagram of Circuit:

Even Parity generator

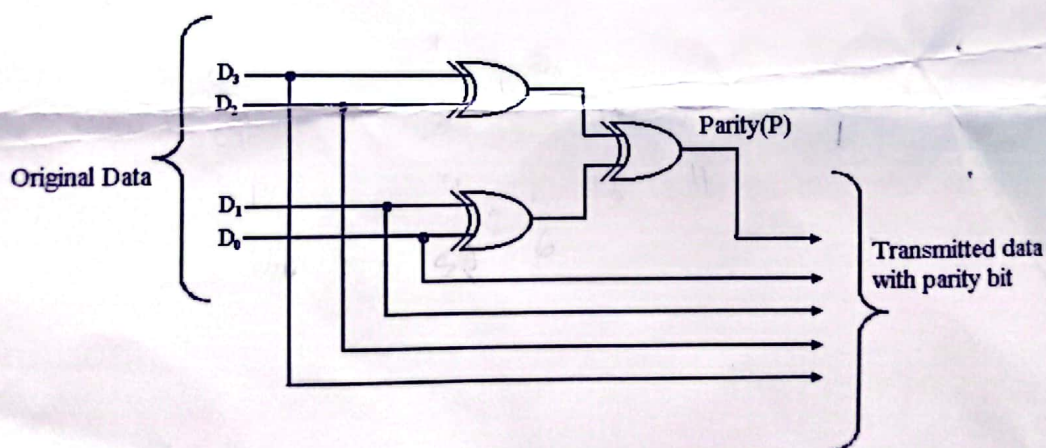

Even Parity Checker

 

Procedure:

- Construct the Circuit of Figure 1, on the breadboard of AT-700.
- Remember each IC's pin 14 connected to "+5V" position of DC Power Supply of AT-700, and pin 7 connected to "GND" position.
- Connect the inputs to Data switches and outputs to any position of LED Display.
- Determine the parity generator's output for each of the following sets of input data, $D_3D_2D_1D_0$; (a) 0111; (b) 1001; (c) 0000; (d) 0100
- Determine the parity checker's output for each of the following sets of data from the transmitter

P	D_3	D_2	D_1	D_0	Error (E)
0	1	0	1	0	
1	1	1	1	0	
1	1	1	1	1	
1	0	0	0	0	

Report:

The report should cover the followings

1. Name of the Experiment
2. Objective
3. Required Components and Equipments
4. Experimental Setup (You must draw the diagrams)
5. Results in Tabulated form.
6. Discussions (Explanation of the results)

①

Name of the Experiment:

Parity Generator and Checker

Objective:


- To design and implement an Even parity Generator and Even parity checker using XOR gates (IC-7486).

Required Components and Equipments:


1. AT-700 Portable Analog/Digital Laboratory
2. 7400 X 3

Experimental Setup:

Even parity Generator

 

Even Parity Checker

 

Results in Tabulated form:

Even parity ~~Generator's~~ Generator's output:

D_3	D_2	D_1	D_0	Output = P	A	B	R
0	1	1	1	1	1	0	1
1	0	0	1	0	1	1	0
0	0	0	0	0	0	0	0
0	1	0	0	1	1	0	1

Even parity Checker's output

P	D_3	D_2	D_1	D_0	A	B	R	Error(E)
0	1	0	1	0	1	1	0	0
1	1	1	1	0	0	1	1	0
1	1	1	1	1	0	0	0	1
1	0	0	0	0	0	0	0	1

(3)

Discussions:

For the Even parity Generator, ~~D_3, D_2, D_1~~ the inputs are D_3, D_2, D_1 and D_0 . The output is R . If the inputs are an odd number of 1, the output (R) comes out to be 1 in order to make it even. Otherwise, 0 is produced as the output (R).

The XOR gate in the even parity checker takes two inputs: ~~R and the a different input~~ R and an external input, P . It compares the two inputs and checks if R and P are ~~the same~~ ^{equivalent}. If they are ^{equivalent} ~~the same~~, 0 (no error) is produced as the output, otherwise, 1 (error) is produced the output.

This is similar to how we check if ~~a sender's output is~~ ~~equivalent to a receiver's input~~ a sender's ~~data~~ ^{data} is equivalent to the data that ^{is} ~~received~~ by a receiver.