

CSE 260

LAB Experiment-07

Submitted by : (Group-1) (Section-18)

1. ANIKA TOUSHIN SINTHIA
ID - 24311251
2. TASNIM RAHMAN MOUMITA
ID - 22301689
3. TASNOVA RAHMAN
ID - 24341260
4. AYSHA SIDDIQUA TITHI
ID - 22301667

Date of Submission : 25.09.2024

Name of the experiment : Design a circuit that outputs 2's complement of a 3 bit number using encoder & decoder.


Objective :

- understand the hardware system to calculate 2's complement of a 3 bit number.
- Obtain ideas about encoders and decoders.

Required Components and Equipments :

- IC 7415 138 [decoder]
- IC 74LS 148 [encoder]
- Jumper wires
- Breadboard.

Experimental setup :

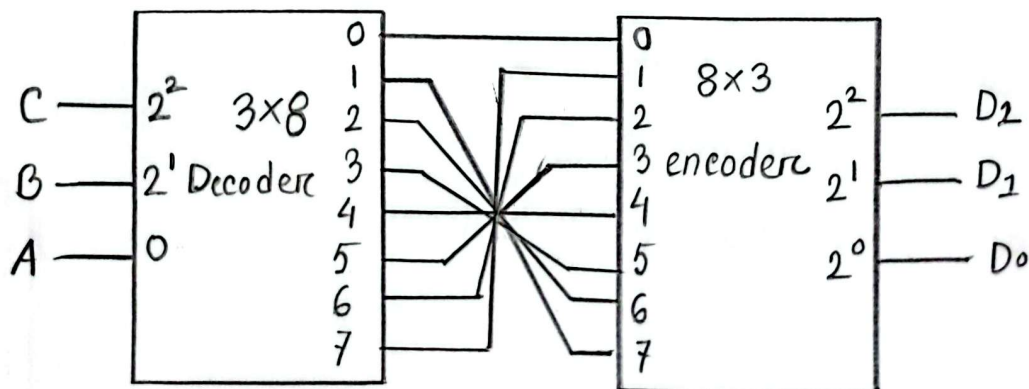

Truth Table for 2's complement output :

Inputs				Outputs				Active low output			Output line connection	
Minterm	C	B	A	Minterm	D ₂	D ₁	D ₀	D ₂	D ₁	D ₀	Decoder	Encoder
0	0	0	0	0	0	0	0	1	1	1	0	0
1	0	0	1	1	1	1	1	0	0	0	1	7
2	0	1	0	2	1	1	0	0	0	1	2	6
3	0	1	1	3	1	0	1	0	1	0	3	5
4	1	0	0	4	0	0	0	0	1	1	4	4
5	1	0	1	5	0	1	1	1	0	0	5	3
6	1	1	0	6	0	1	0	1	1	1	6	2
7	1	1	1	7	0	0	1	1	1	0	7	1

Results and Discussions:

(a)

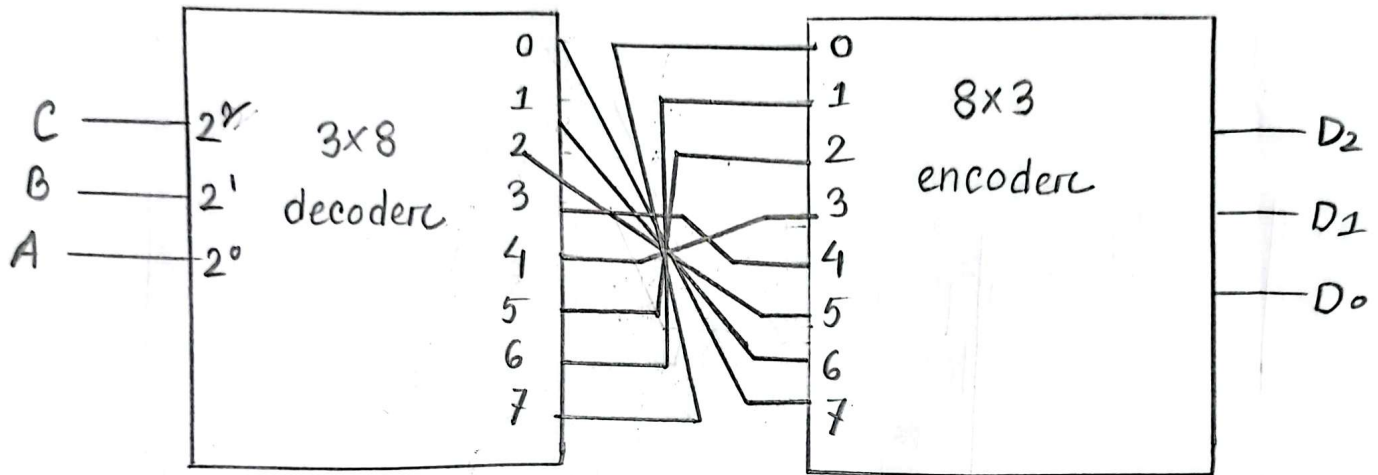


Figure: circuit diagram with encoder and decoder that will output the 1's complement of 3 bit number.

(b) Yes, we can implement a code converter with encoder and decoder.

For example, '3' is given in the input of 3x8 decoder (011) and the 3rd line in the output activates. The 3rd line in the output of the 3x8 decoder needs to be connected with the 6th line of the input of the 8x3 encoder.

Thus, BCD is connected to excess 3 using 3x8 decoder and 8x3 encoder.