


CSE260 Summer 2024

Assignment 04

This assignment must be hand-written. Show ALL steps in ALL questions.

Question 1:

Given the state diagram as follows, get the sequential circuit using SR flipflop

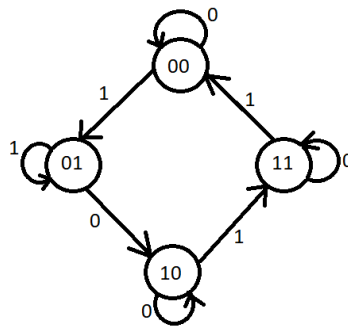

Question 2:

3->4->6->10->12->13->15->3

- Implement the given counter using JK flip-flop.
- Implement the given counter using T flip-flop.

Question 3:

Implement 2 bits up/down counter using D flip flop

Question 4:

Draw the state diagram for the given circuit.

