

## Assignment 2

Total: 50

**Deadline: March 3, 2025**

**This assignment must be hand-written. Show ALL steps in ALL questions.**

1. [5 Marks] **Simplify** the following boolean expression:

$$(A + B)(A+B)(A+C)$$

2. [5 Marks] **Find** the complement of the following expression:

$$(x' + y + z')(x' + y')(x + z')$$

3. [5 Marks] **Draw** the following functions using NAND gates only:

$$F(A,B,C,D) = (A'B'CD' + A'D + (B+D'))$$

**NB:** You can't simplify the above function. You have to draw based on the function given in question.

4. [5 Marks] **Draw** the following functions using NOR gates only:

$$F(A,B,C,D) = (AB'C'D' + AD + (B+D'))$$

**NB:** You can't simplify the above function. You have to draw based on the function given in question.

5. [5 + 5 + 5 Marks] **Find** out Canonical SOP and POS for the following: (Do not use truth table)

a.  $F(A,B,C) = AB+BC'$

b.  $F(A,B,C,D) = A+ B'CD'$

c.  $F(A,B,C,D,E) = AB+CDE$

6. [5 Marks] **Simplify** the following boolean equation using the laws of boolean algebra and implement the simplified function using only NOR gates:

$$F(a,b,c,d) = \sum(8, 9, 10, 11, 13, 15)$$

7. [5 + 5 Marks] **Simplify** the following boolean equation using the laws of boolean algebra and implement the simplified function using only NAND gates:

a.  $F(a,b,c,d) = \sum(8, 9, 0, 11, 7, 15)$

b.  $F(a,b,c,d) = \sum(5, 8, 9, 12, 15)$