

CSE 250

Submitted by :- Tasnim Rahman Moumita



ID :- 22301689

Section :- 28

Date of submission :- 13.10.2023

Assignment ~ 01

Answers to the Question NO-01

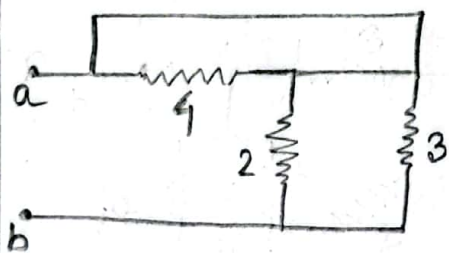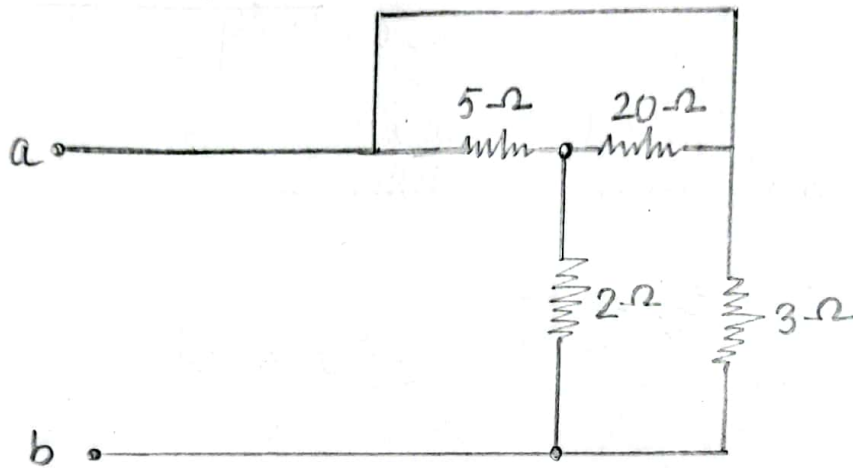

Here,

$$20 \parallel 5 = \frac{1}{\frac{1}{20} + \frac{1}{5}}$$
$$= \frac{1}{\frac{1}{4}}$$

$$\therefore 20 \parallel 5 = 4 \text{ (parallel)}$$

$$\text{Now, } 4 \Omega + 2 \Omega = 6 \Omega \text{ (series)}$$

$$\therefore \frac{1}{R_{ab}} = \frac{1}{3} + \frac{1}{6} \Omega$$

$$\Rightarrow R_{ab} = 2 \Omega \text{ (Ans.)}$$

Here,



$$R_1 = 5 \Omega$$

$$R_2 = 20 \Omega$$

$$R_3 = 2 \Omega$$

$$R_4 = 3 \Omega$$

Answer to the Question NO - 02

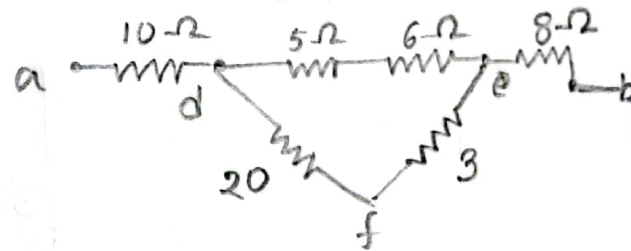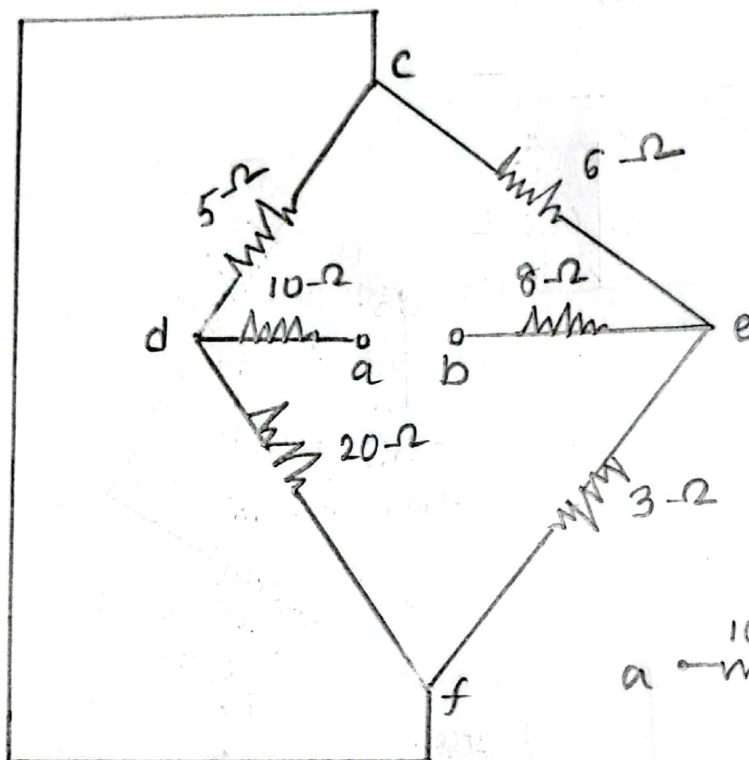

Here,

$$5\ \Omega \parallel 20\ \Omega = 4\ \Omega$$


$$6\ \Omega \parallel 3\ \Omega = 2\ \Omega$$

c and f point are at same,

\therefore in series it will make $= 10 + 4 + 2 + 8 = 24\ \Omega$

$\therefore R_{ab} = 24\ \Omega$ (Ans:)

Answer to the Question NO- 03 (a)

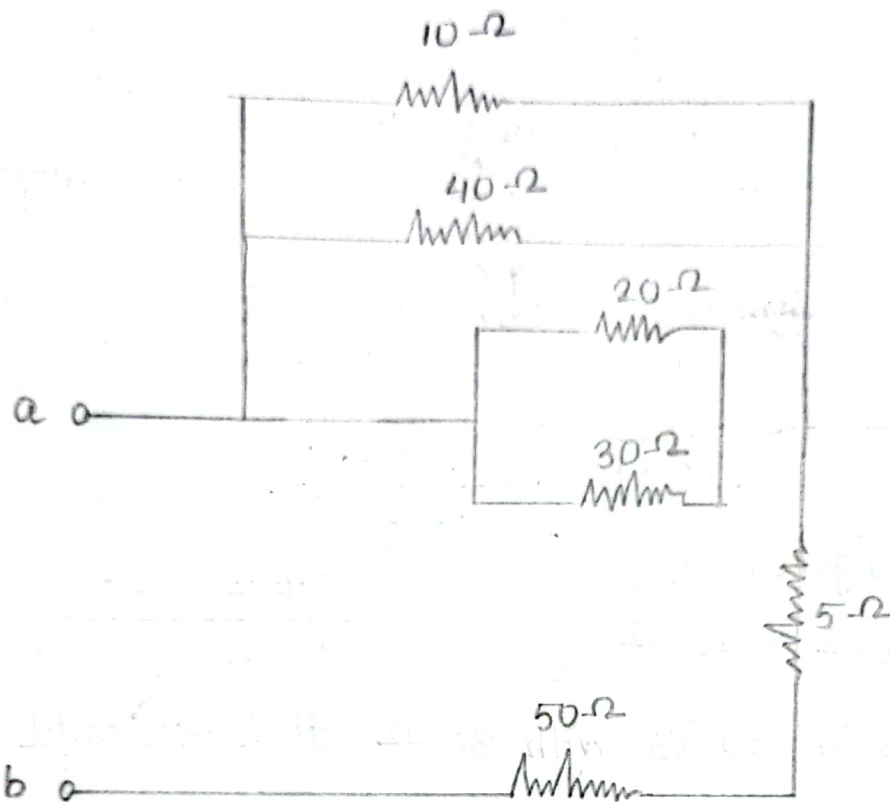

$10\text{-}\Omega$ and $40\text{-}\Omega$ are in parallel

$$\therefore 10 \parallel 40 = \frac{1}{10} + \frac{1}{40}$$

$$\Rightarrow 10 \parallel 40 = 8$$

Again,

$$20 \parallel 30 = 12$$

And,



$$8 \parallel 12 = 4.8$$

$$\therefore R_{ab} = 5 + 50 + 4.8$$

$$= 59.8\text{-}\Omega$$

(Ans:-)

Answer to the Question NO-3(b)

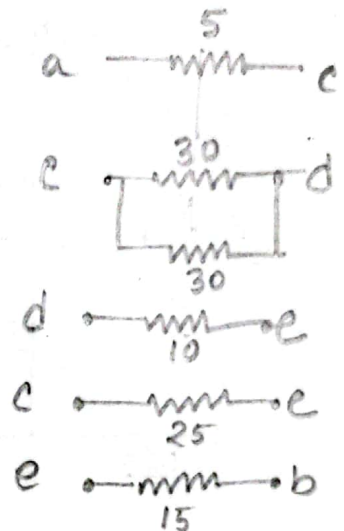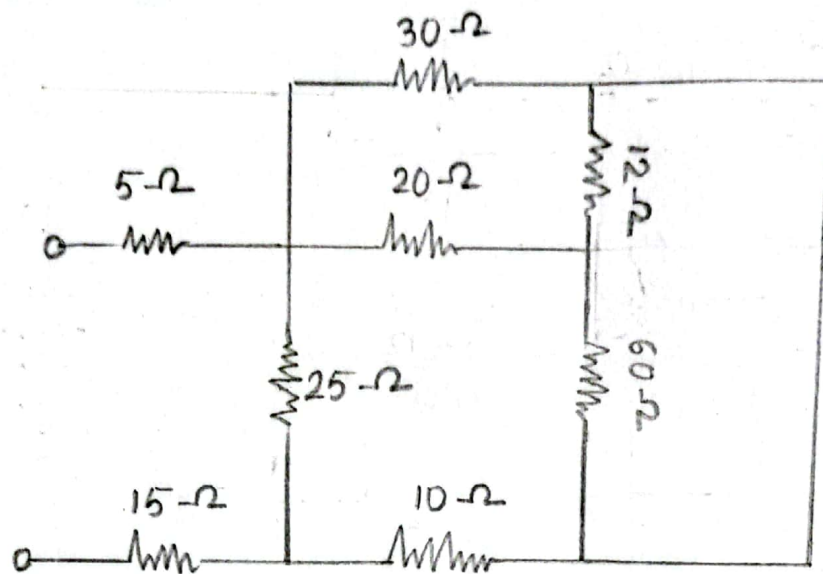

In this given figure,

$$12\ \Omega \parallel 60\ \Omega = 10\ \Omega$$


and $20\ \Omega$ is in series with $30\ \Omega$. It is parallel with $30\ \Omega$.

$$\therefore 30 \parallel 30 = 15\ \Omega$$


$$\text{and } 25 \parallel (15 + 10) = 12.5\ \Omega$$

$$\therefore R = 5 + 12.5 + 15\ \Omega$$

$$= 32.5\ \Omega \quad (\text{Ans:})$$

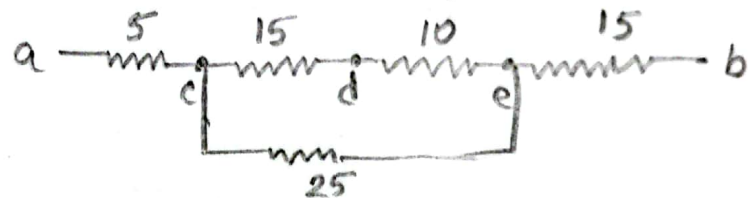

Answer to the Question NO. - 04

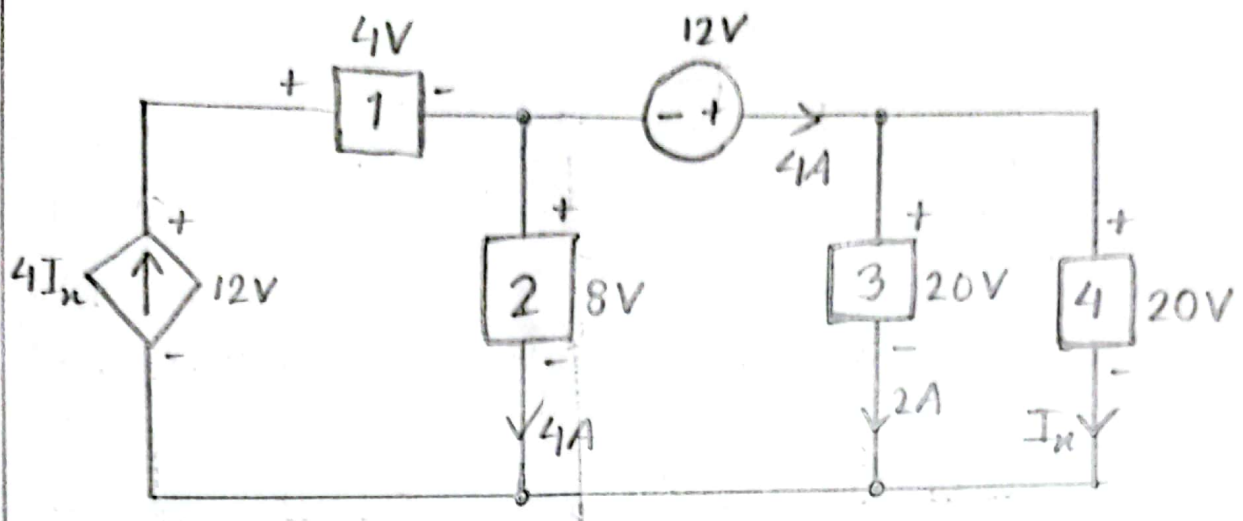

We know,

$$P = VI$$

$$P_1 = 4 \times 4I_x = 4 \times 4 \times I_x = 4 \times 8 = 32 \Omega$$

$$P_2 = 8 \times 4 = 32 \text{ W}$$

$$P = -12 \times 4 = -48 \text{ W}$$

$$P_3 = 20 \times 2 = 40 \text{ W}$$

$$P_4 = 20 \times I_x = 40 \text{ (W)}$$

$$V = IR$$

$$\Rightarrow R = \frac{V}{I}$$


$$P_4 = 20 \times I_x$$

$$\Rightarrow 40 = 20 \times I_x$$

$$\therefore I_x = 2 \text{ A}$$

$$\therefore I_x = 2 \text{ A} \quad (\text{Ans:})$$

Answer to the Question NO-05

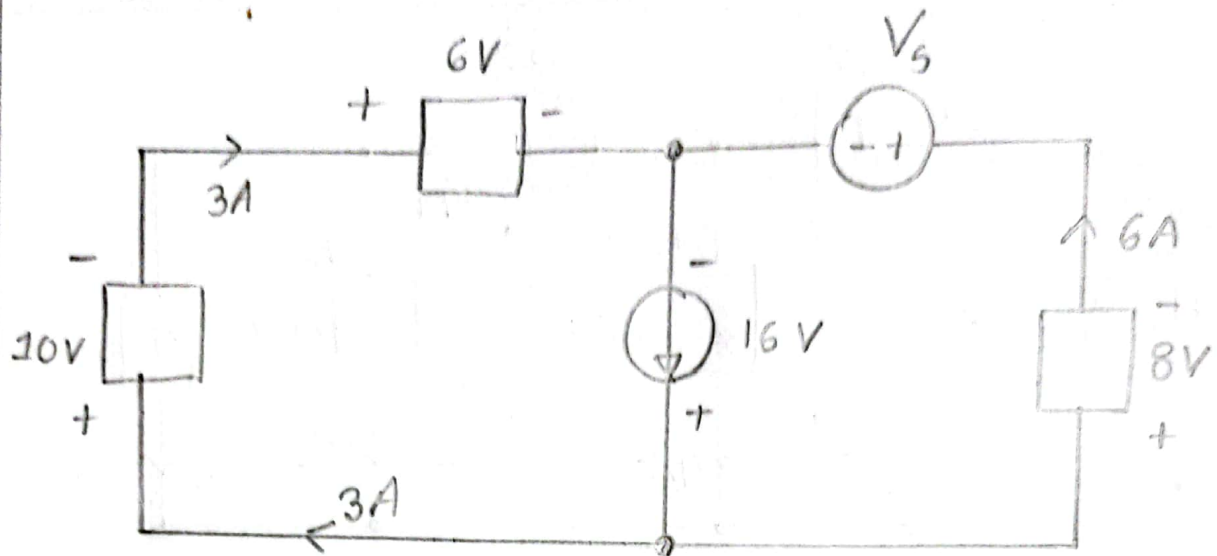

For the given circuit,

$$P_{10V} = 10 \times 3 = 30W$$

$$P_{6V} = 6 \times 3 = 18W$$

$$P_{9A} = 16 \times -9 = -144W$$

$$P_{V_s} = V_s \times 6 = 6V_s W$$

$$P_{8V} = (8) \times 6 = 48W$$

For this, one source supplies power (the element with the negative power value), and the power absorbed by the other elements must equal each other.

$$\therefore -144 + 30 + 18 + 6V_s + 48 = 0$$


$$\Rightarrow 6V_s = 48$$

$$\Rightarrow V_s = 8V$$


$$\therefore P_{V_s} = 8 \times 6 = 48W$$

(Ans.)

Answer to the Question NO-06

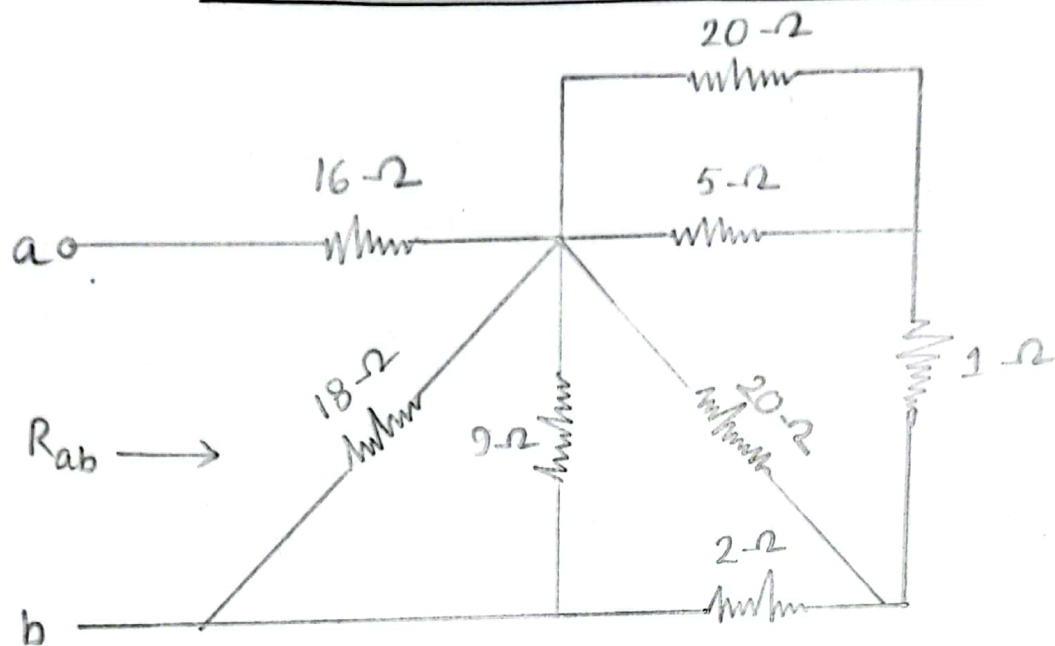

simplifying the given circuit,

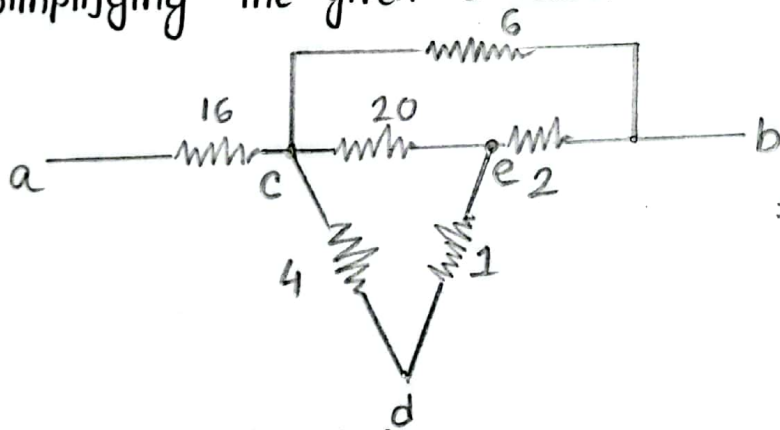

$$4 + 1 = 5 \text{ } \Omega \text{ (series)}$$

$$20 \parallel 5 = 4 \text{ } \Omega \text{ (parallel)}$$



$$\therefore R_{ab} = 16 + \{(4+2) \parallel 6\}$$

$$= 16 + 3$$


$$= 19 \text{ } \Omega$$

$$\therefore R_{ab} = 19 \text{ } \Omega$$

(Ans:)

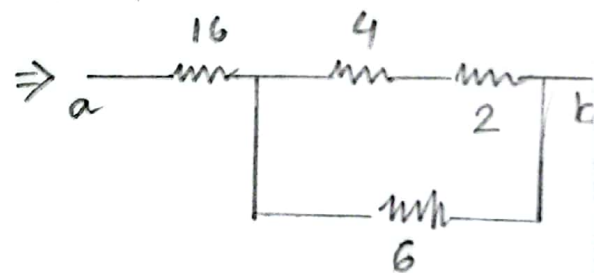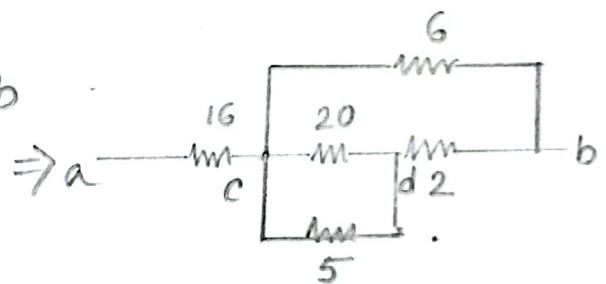

Answer to the Question NO-07

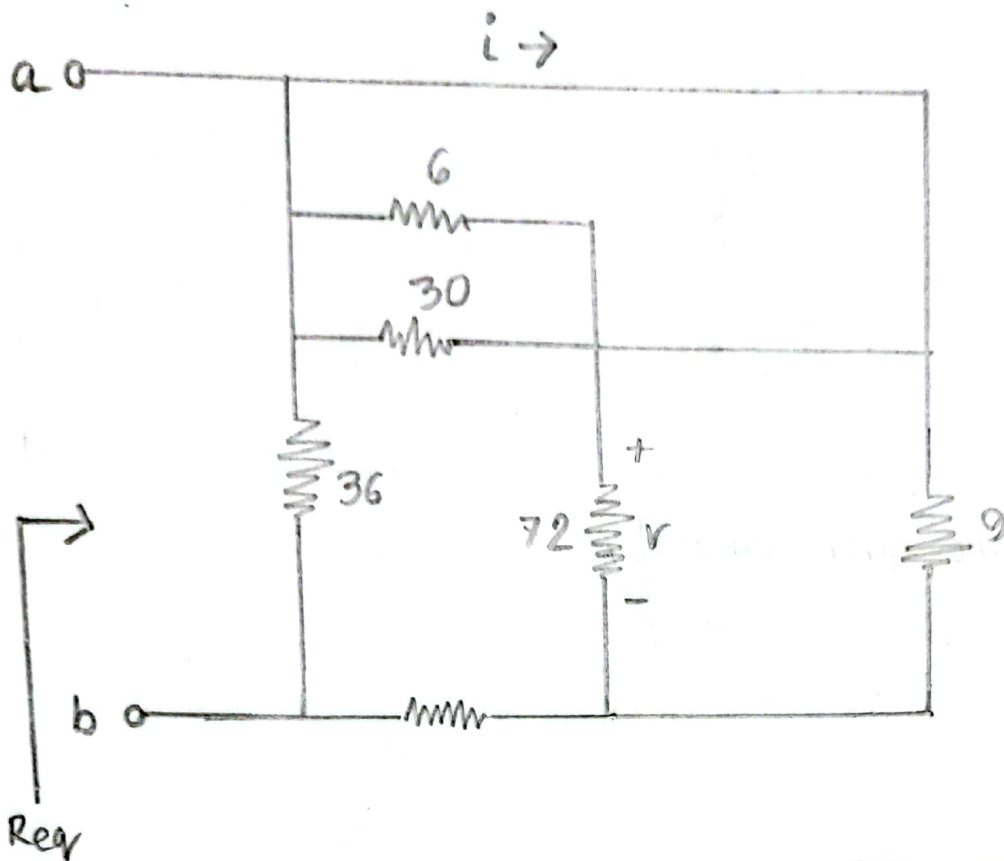

6 Ω and 30 Ω are in parallel.



$$\therefore 6 \parallel 30 = \frac{1}{6} + \frac{1}{30}$$

$$\therefore 6 \parallel 30 = 5$$



Again, 72 Ω and 9 Ω are in parallel.

$$\therefore 72 \parallel 9 = 8 \Omega$$

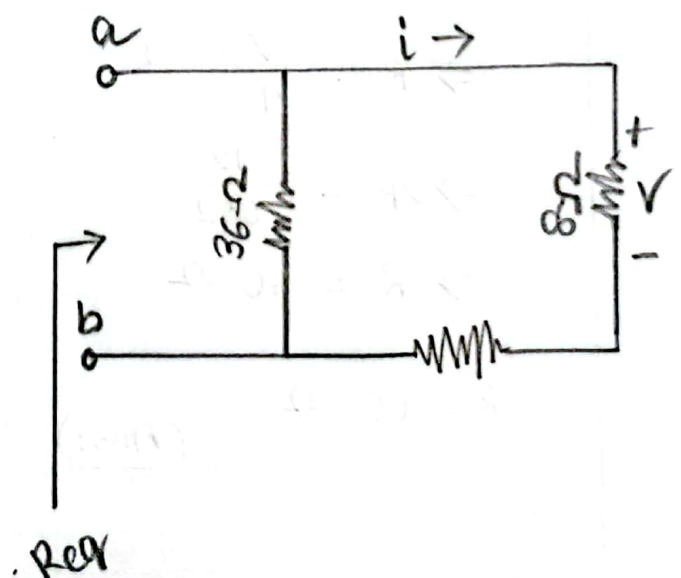
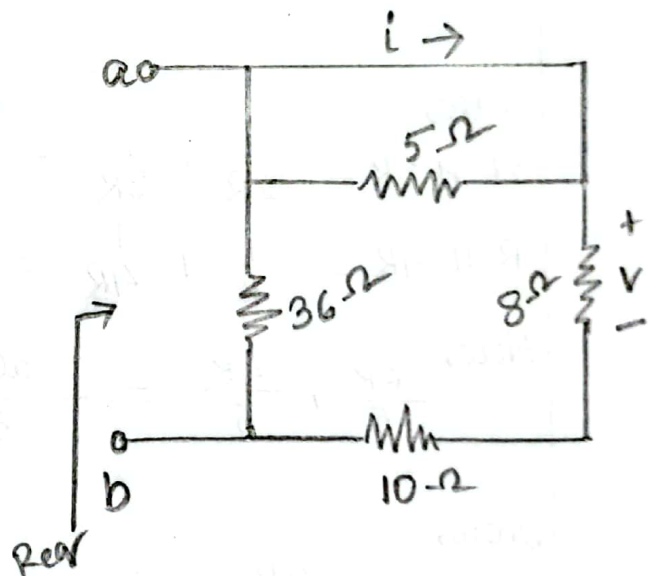
$$\therefore R_{eq} = 36 \parallel (8 + 10) = 12 \Omega$$



Answer to the Question NO-08

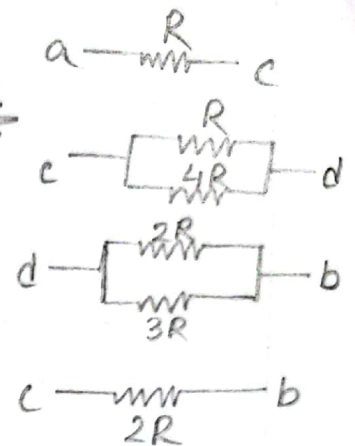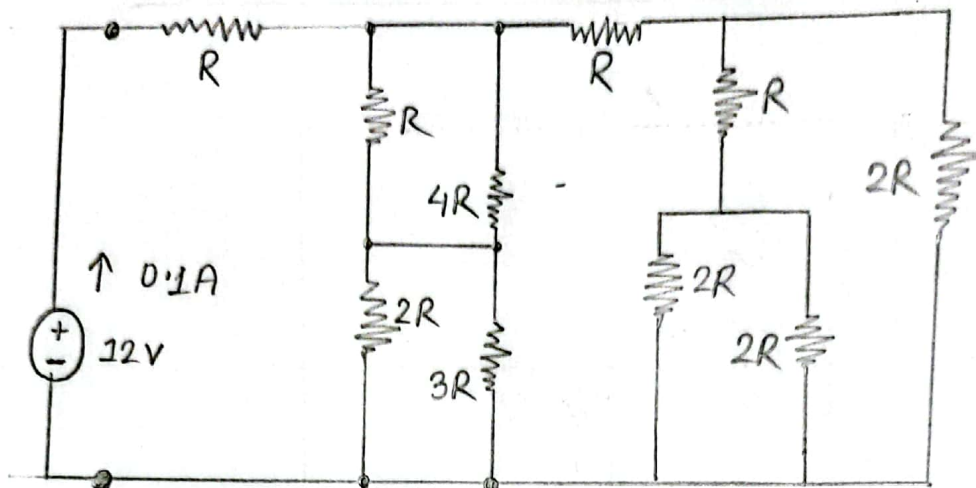

Simplifying the given circuit,

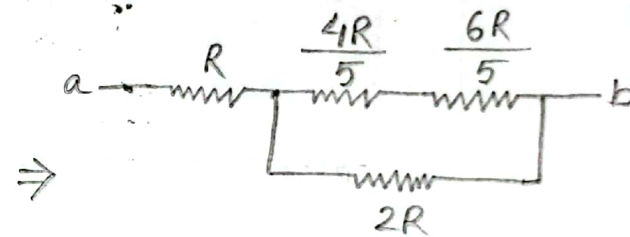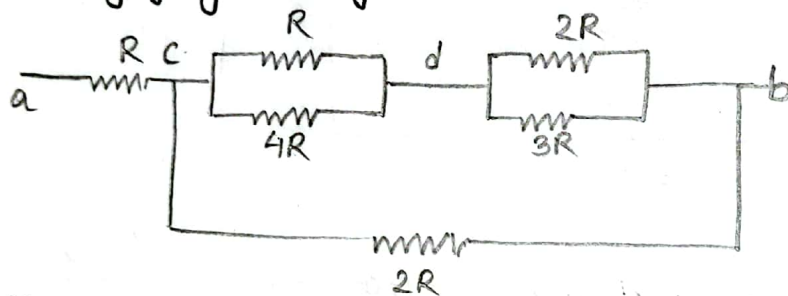

Here,

$$2R \parallel 3R = \frac{1}{\frac{1}{2R} + \frac{1}{3R}} = \frac{2R \times 3R}{2R + 3R} = \frac{6R^2}{5R} = \frac{6R}{5} \text{ (parallel)}$$

$$R \parallel 4R = \frac{1}{\frac{1}{R} + \frac{1}{4R}} = \frac{R \times 4R}{R + 4R} = \frac{4R^2}{5R} = \frac{4R}{5} \text{ (parallel)}$$

$$\text{Now, } \frac{6R}{5} + \frac{4R}{5} = \frac{10R}{5} = 2R \text{ (series)}$$

Now,

$$V = IR$$

$$\Rightarrow R = \frac{V}{I}$$


$$\Rightarrow 2R = \frac{12}{0.1}$$

$$\Rightarrow R = 60 \Omega$$

$$\therefore R = 60 \Omega$$


(Ans:)

Answer to the Question NO-09

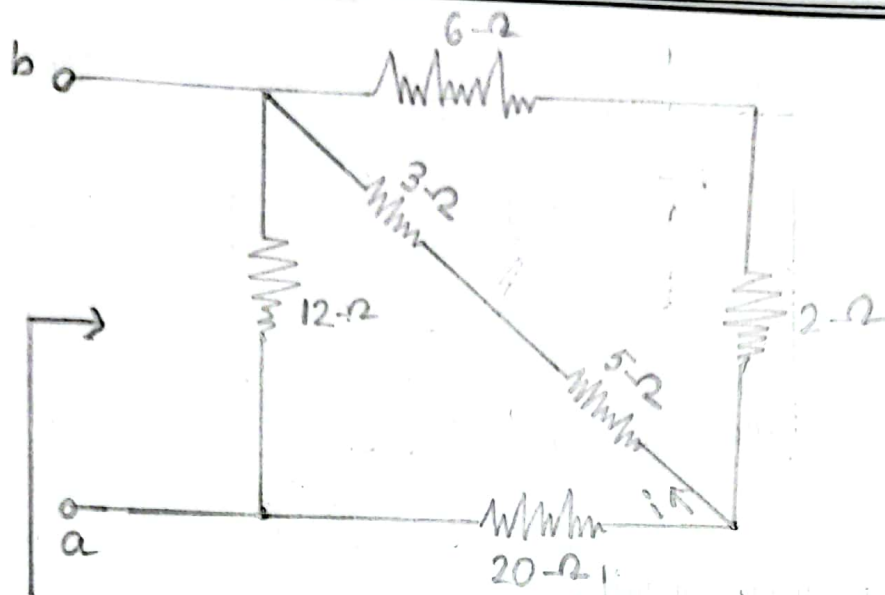

$R_{eq\ a-b}$

simplifying the given circuit,

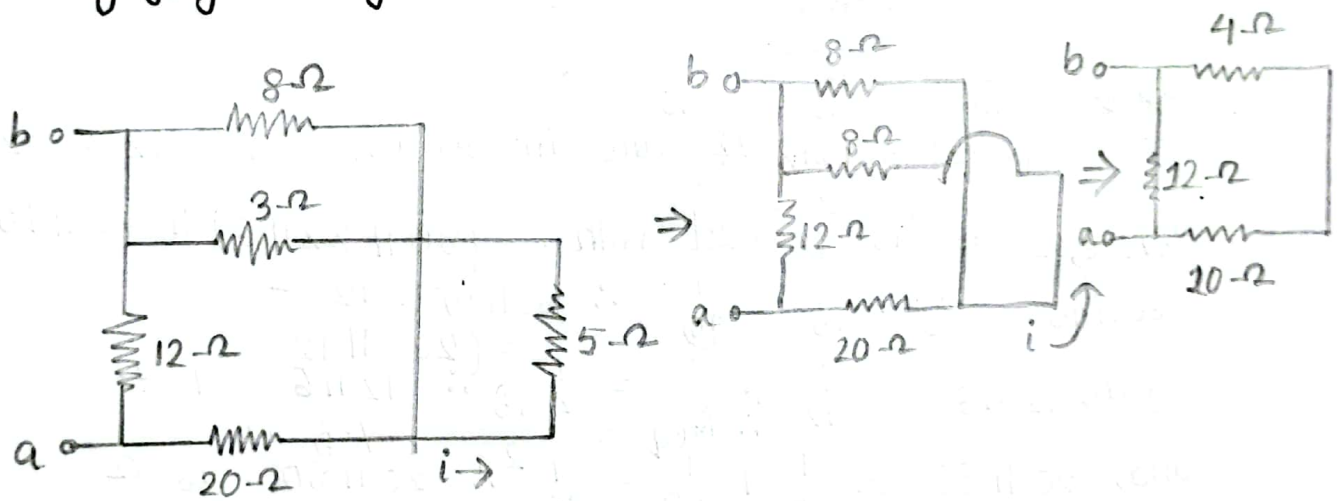


$$\text{For, } R_{eq} = 24 \parallel 12 = \frac{24 \times 12}{24 + 12} = 8\Omega \quad (\text{Ans:})$$

for voltage division,

$$V_R = 40 \left(\frac{20}{20 + 4} \right) = \frac{100}{3} \text{ V}$$


$$\therefore I_R = \frac{\frac{100}{3}}{20} = \frac{5}{3} \text{ A}$$
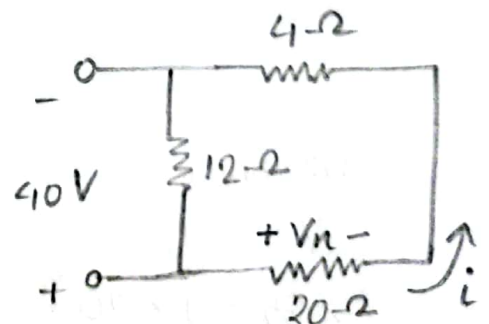
$$\therefore \text{current division, } i = I_R \left(\frac{8}{8 + 8} \right) = \frac{5}{6} = 0.83 \text{ A} \quad (\text{Ans:})$$





Answer to the Question NO - 10

Given,

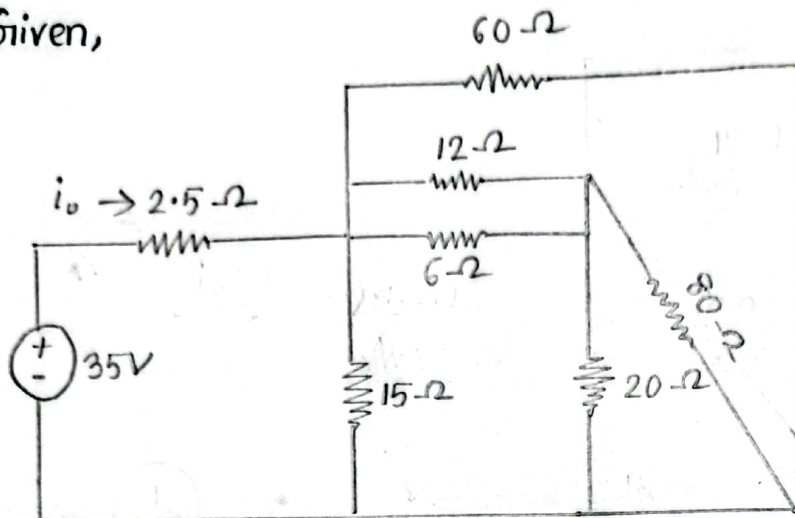

simplifying the given circuit,

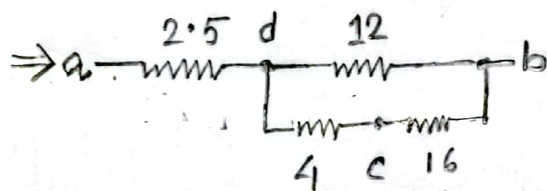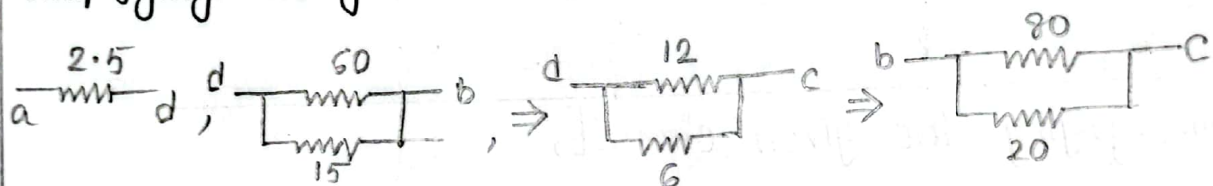

Here,

$$60 \parallel 15 = \frac{1}{60} + \frac{1}{15} = \frac{1}{12} \quad \therefore 60 \parallel 15 = 12 \, \Omega$$

$$\text{again, } 12 \parallel 6 = \frac{1}{12} + \frac{1}{6} = \frac{1}{4} \quad \therefore 12 \parallel 6 = 4 \, \Omega$$

$$\text{and, } 20 \parallel 80 = \frac{1}{20} + \frac{1}{80} = \frac{1}{16} \quad \therefore 20 \parallel 80 = 16 \, \Omega$$

$$\text{Now, } 2.5 + (12 \parallel 20) = 2.5 + \left(\frac{1}{12} + \frac{1}{20} \right)$$

$$= 2.5 + 7.5$$

$$= 10 \, \Omega = R_{eq} \quad (\text{Ans:})$$

We know,

$$V = IR$$

$$\Rightarrow 35 = I \times 10$$

$$\Rightarrow I = 3.5 \, A \quad (\text{Ans:})$$