

CSE 251

Assignment — 01

Tasnim Rahman Moumita


ID — 22301689

Section — 18

Date of submission — 07.02.2024


Answer to the Question NO - 1(a)

alternate representation :-

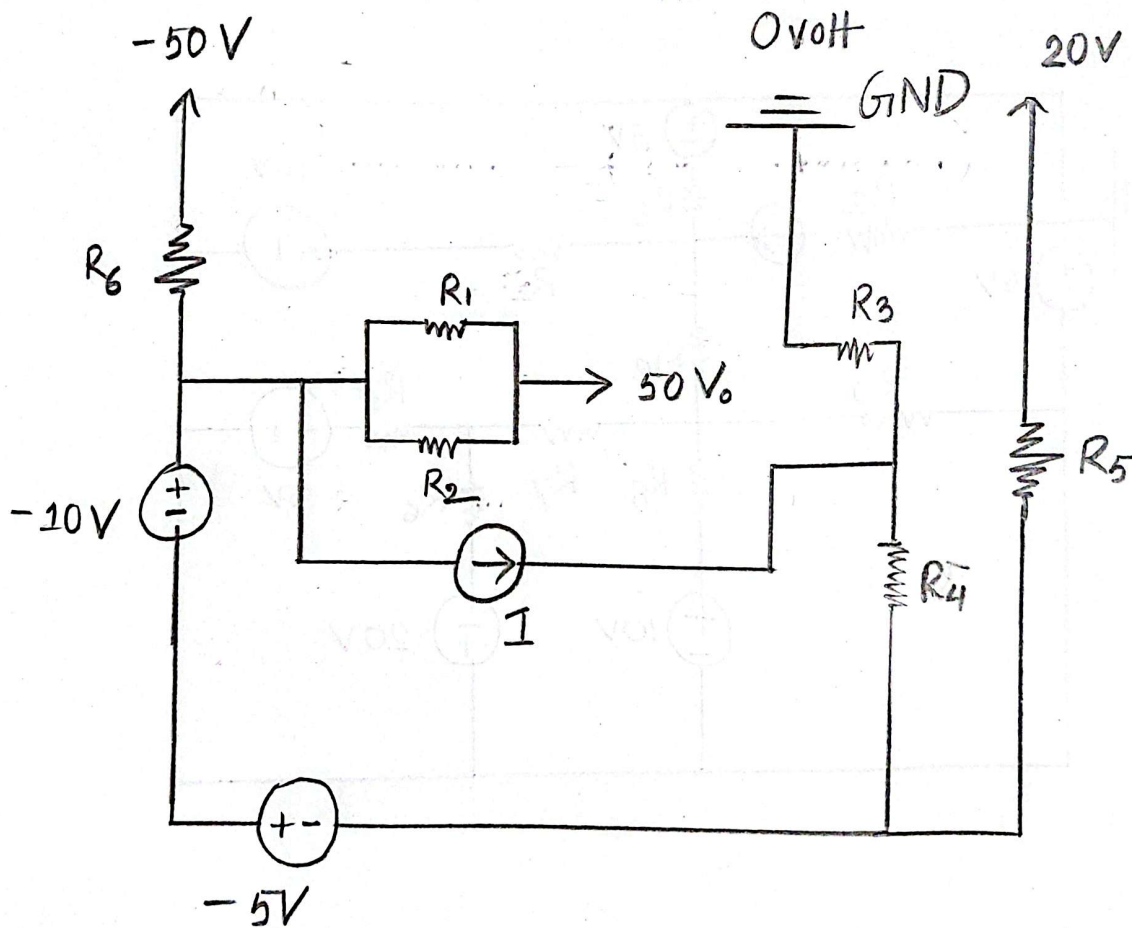


Answer to the Question NO-1(B)

Alternate representation:-

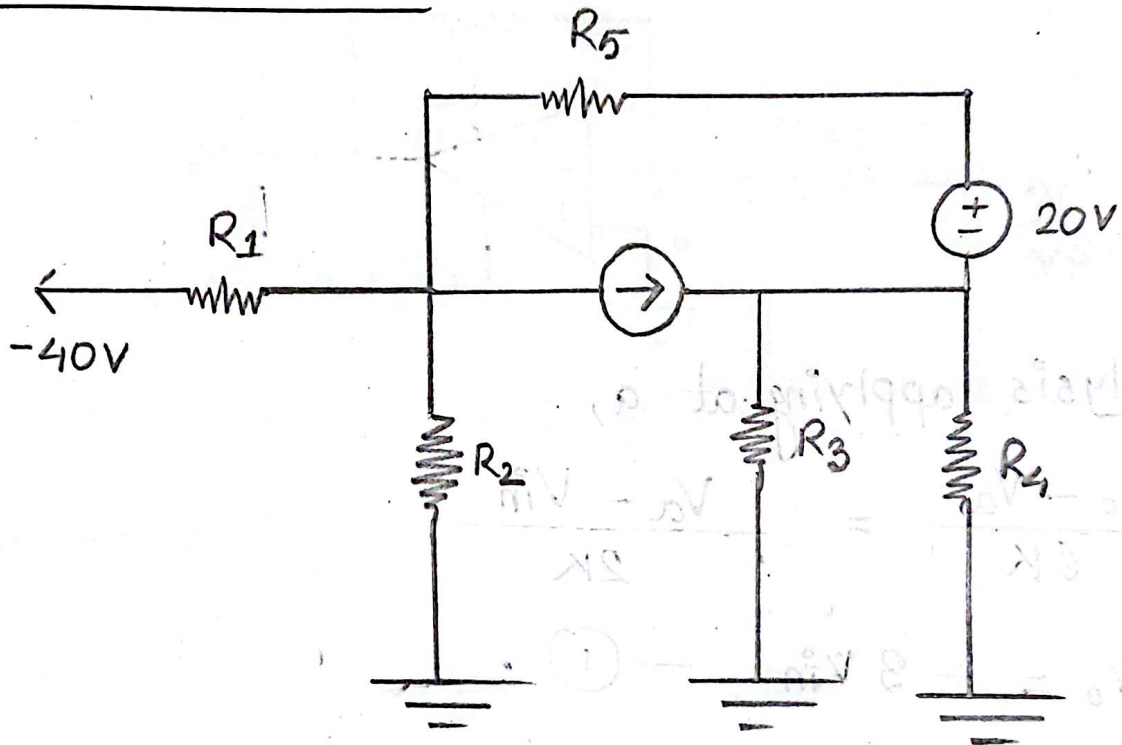


Answer to the Question NO - 02

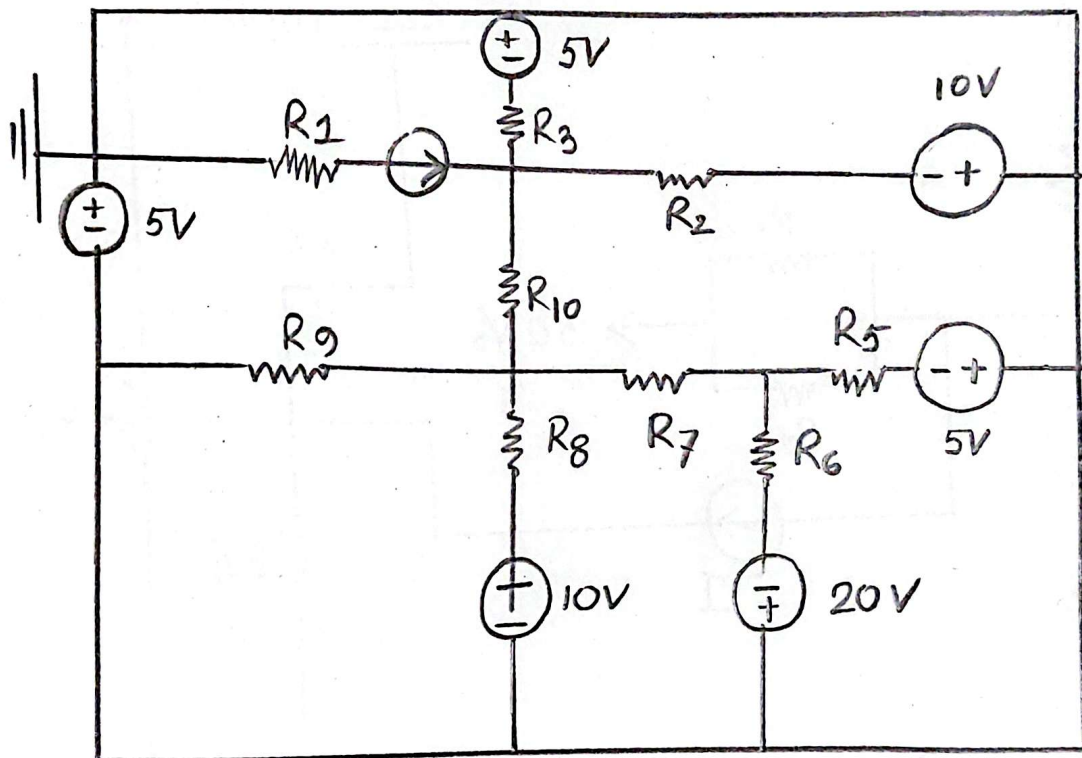
Full form representation of the given circuit:-



Answer to the Q. NO-03 (A)

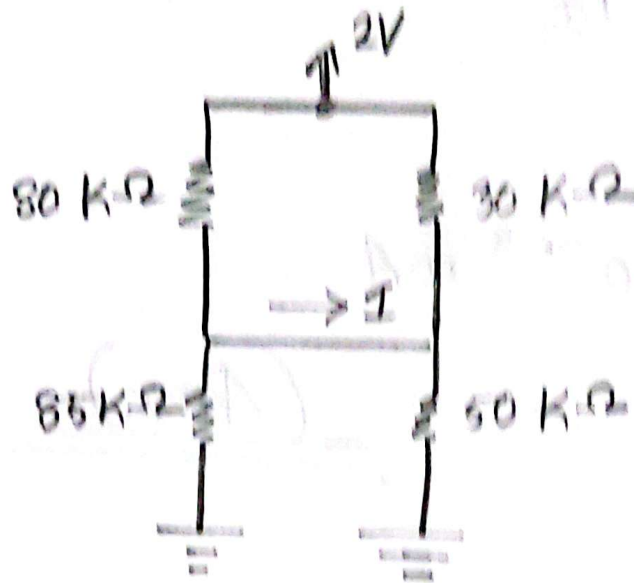

Answer to the Q. NO - 3 (B)

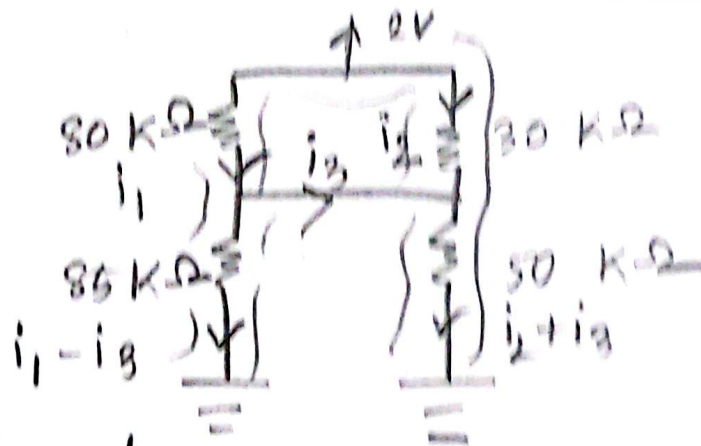

Applying Formula,

$$80 i_1 + 85 i_1 - 85 i_3 = 2$$

$$\Rightarrow 165 i_1 - 85 i_3 = 2 \quad \text{--- (I)}$$

$$\text{Again, } 50 i_2 + 50 i_2 + 80 i_1 = 2 \quad \text{--- (II)}$$

$$\text{And, } 20 i_2 + 50 i_2 + 50 i_2 = 2 \quad \text{--- (III)}$$



50+

ART.O.7

Clonatil[™]
clonazepam USP

(A) 80 - 0.01 mA off of current

$$i_1 = 0.01 \text{ mA} = i_2$$

$$i_2 = 0.03 \text{ mA}$$


$$i_3 = -3.7 \times 10^{-3} \text{ mA}$$

(Ans:)

(B) 80 - 0.01 mA off of current

Answer to the Question NO-04

Given circuit,

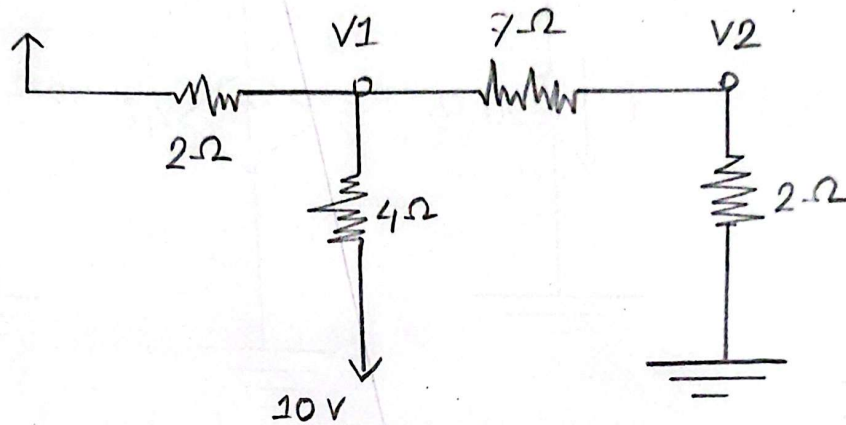

In node-1 :-

$$\begin{aligned} V_1 \left(\frac{1}{2} + \frac{1}{4} + \frac{1}{7} \right) - \frac{10}{2} - \frac{10}{4} - \frac{V_2}{7} &= 0 \\ \Rightarrow V_1 \left(\frac{1}{2} + \frac{1}{4} + \frac{1}{7} \right) &= \frac{10}{2} + \frac{10}{4} + \frac{V_2}{7} \\ \Rightarrow V_1 \left(\frac{1}{2} + \frac{1}{4} + \frac{1}{7} \right) - \frac{V_2}{7} &= \frac{15}{2} \quad \text{--- (I)} \end{aligned}$$

In node-2 :-

$$V_2 \left(\frac{1}{7} + \frac{1}{2} \right) - \frac{V_1}{7} = 0 \quad \text{--- (II)}$$

By solving (I) and (II) \Rightarrow


$$V_1 = 8.70 \text{ V}$$

$$V_2 = 1.94 \text{ V}$$

(Ans:)

Answer to the Question NO - 05

Given circuit,

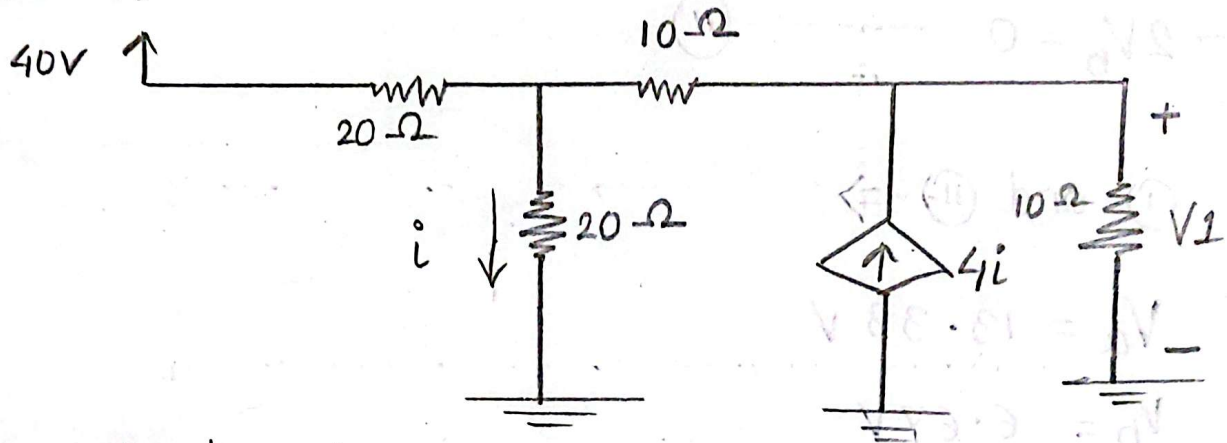

Applying KCL at node V_a ,

$$V_a \left(\frac{1}{20} + \frac{1}{20} + \frac{1}{10} \right) - \frac{40}{20} - \frac{0}{20} - \frac{V_b}{10} = 0$$

$$\Rightarrow V_a \left(\frac{1+1+2}{20} \right) - 2 - \frac{V_b}{10} = 0$$

$$\Rightarrow V_a \left(\frac{5}{20} \right) - 2 - \frac{V_b}{10} = 0$$

$$\Rightarrow V_a \left(\frac{1}{5} \right) - \frac{V_b}{10} = 2$$

$$\Rightarrow \frac{2V_a - V_b}{10} = 20 \quad \text{--- (1)}$$

Applying KCL at V_b node,

$$V_b \left(\frac{1}{10} + \frac{1}{10} \right) - \frac{V_a}{10} - \frac{0}{10} - 4i = 0$$

$$\Rightarrow V_b \left(\frac{2}{10} \right) - \frac{V_a}{10} = 4i$$

$$\Rightarrow \frac{2V_b - V_a}{10} = 4 \times \frac{V_a}{20}$$




Healthcare

Clonatil[®]
clonazepam USP

[P.T.O.]

Answer to the Question NO-06

Given,

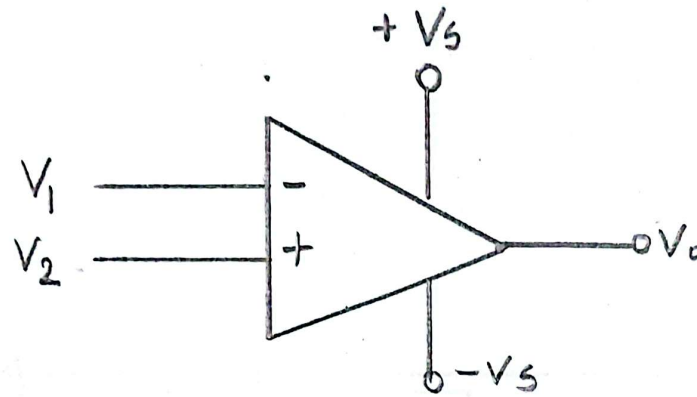

Here,

$$V_1 = 2V$$

V_2 is a sin wave
with an amplitude of
4V

Now,

we will plot the graphs according to the question.

V_1 and V_2 vs t in the same graph:-

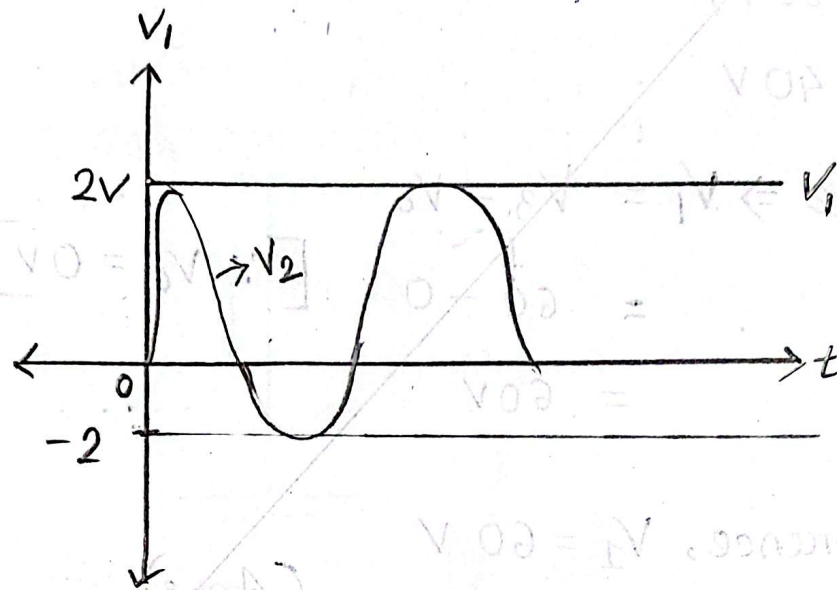


Fig: V_1 and V_2 vs t in the same graph

V_0 vs t graph:-


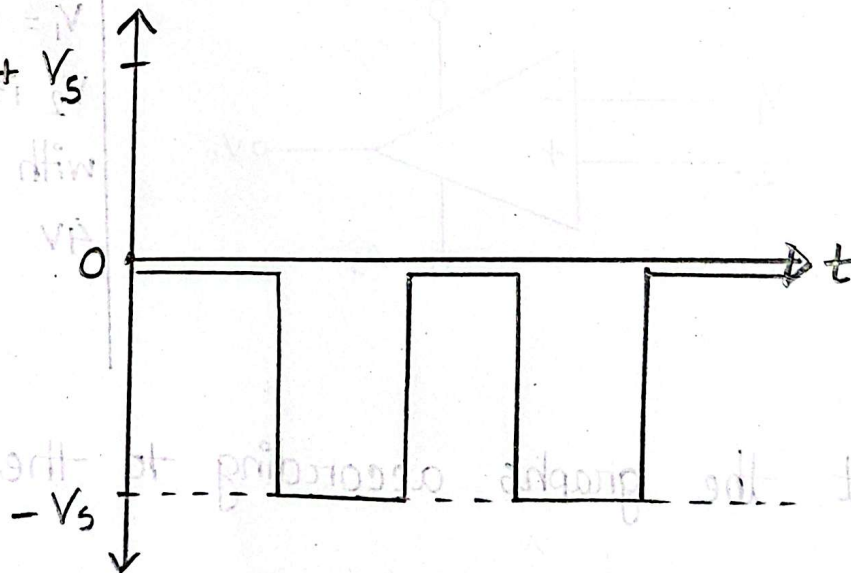


Fig: V_0 vs t graph

Answer to the Q. NO - 7

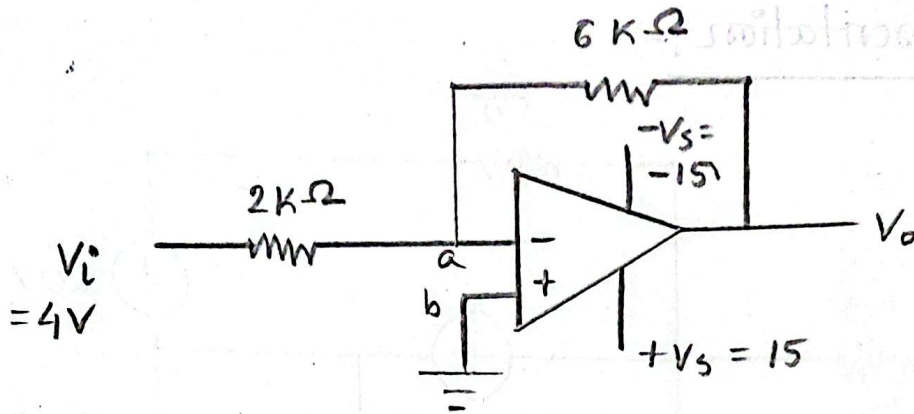

nodal analysis applying at a,

$$\frac{V_o - V_a}{6K} = \frac{V_a - V_{in}}{2K}$$

Now, $\Rightarrow V_o = -3 V_{in}$ — (1)

if $V_{in} = +ve$,

$$-3 V_{in} = -15$$

$$\Rightarrow V_{in} = 5$$

$$\therefore V_o = -15V$$

And, if $V_{in} = -ve$

$$\therefore -3 V_{in} = 15$$

$$\Rightarrow V_{in} = -15V$$

$$\therefore V_o = 15V$$

Now, given, $V_i = 4V$

$$\therefore V_o = -3 \times V_{in}$$

$$= -3 \times 4$$

$$= -12V$$

(Ans:)

Given,

$$V_{in} = 6 \sin(t)$$


$$\therefore V_o = -3 \times V_{in}$$

$$= -3 \times 6 \sin(t)$$

$$= -18 \sin(t).$$

\therefore the value of V_o is greater than $\pm 15V$.

\therefore graph will be,

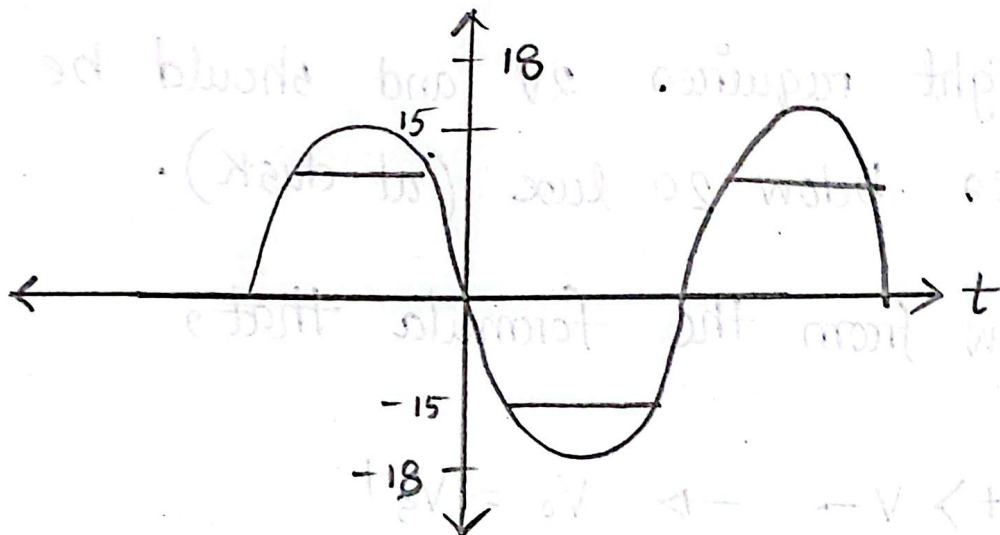

(Ans:)

Answer to the Q. NO-08

Here,
also given,

$$V_{\text{night}} = 0 \text{ lux} \rightarrow 1V$$

$$V_{\text{dusk}} = 20 \text{ lux} \rightarrow 2V$$

$$V_{\text{dawn}} = 80 \text{ lux} \rightarrow 3V$$

Given,
supply voltage
 $= 20V$

As per the Question,

the light requires $2V$ and should be ON if the light goes below 20 lux (at dusk).

We know from the formula that,

$$V_+ > V_- \rightarrow V_o = V_{S+}$$

$$V_- > V_+ \rightarrow V_o = V_{S-}$$

\therefore circuit will be:-

